



**Politecnico  
di Torino**

# DLX Presentation

---

Microelectronic Systems 2021-2022

Alfredo Paolino, Vincenzo Petrolo, Diamante Simone Crescenzo



# Outline

---

- VHDL Design
  - Datapath
  - Instruction memory
  - Data memory
  - Control Unit
- Simulation
- Synthesis
- Physical layout
- Technical report
- Possible improvements

# VHDL Design

- Chosen approach: Bottom-up

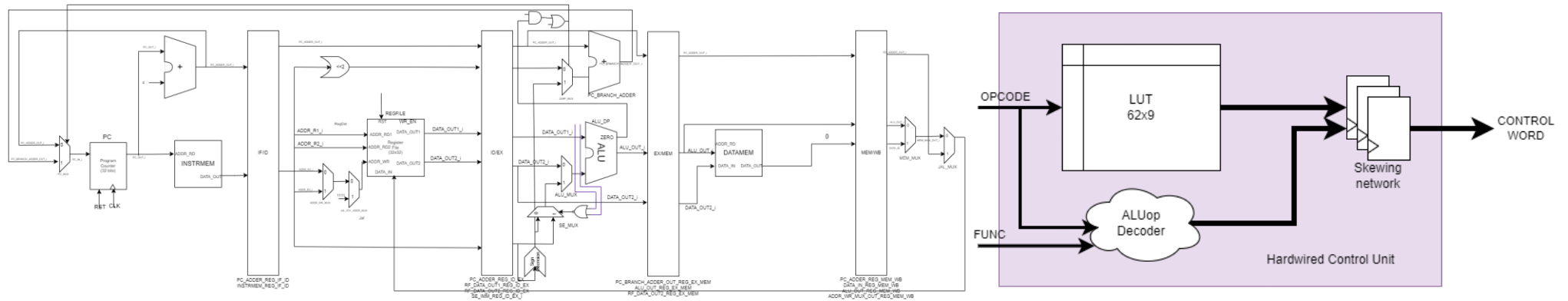 


1

2

3

# VHDL Design (cont.)

- And then we merged them

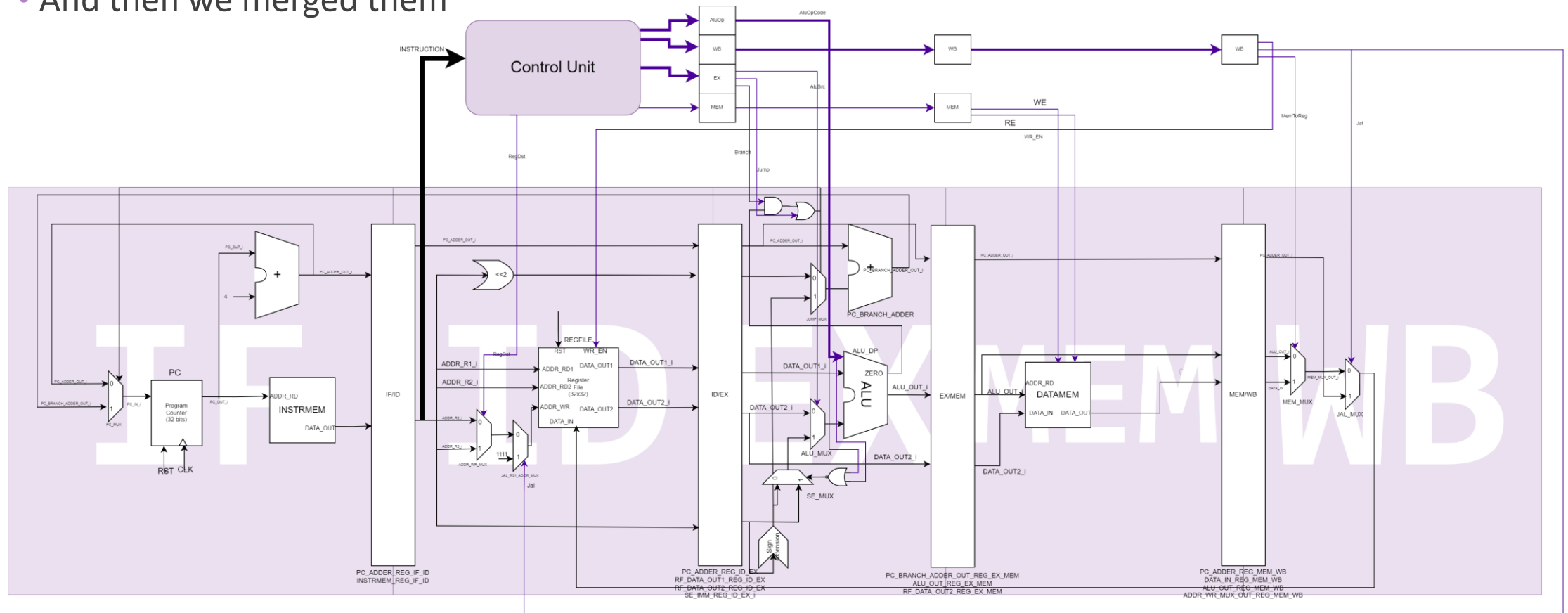

# Datapath


---

- ALU : It is described, using a mixed behavioral-structural description in order to use the Pentium-4 adder in case of additions or subtractions.
- Register File : It is composed of 32 registers and has 2 read ports and 1 write port.
- Adders : Ripple carry adders used for computing next Program Counter.
- Multiplexers : Are used to choose between input sources in the Register File, Program Counter and ALU.
- Pipeline registers : Are used to store the results from previous stage.
 
# Instruction Memory

---


- Size : 2 kB
- Word : 32 bits
- It contains the firmware that is loaded into the microprocessor.
- Asynchronous memory.


 
# Data memory

---


- Size : 2 kB
- Word size: 32 bits
- It stores data coming from registers.
- Asynchronous memory.


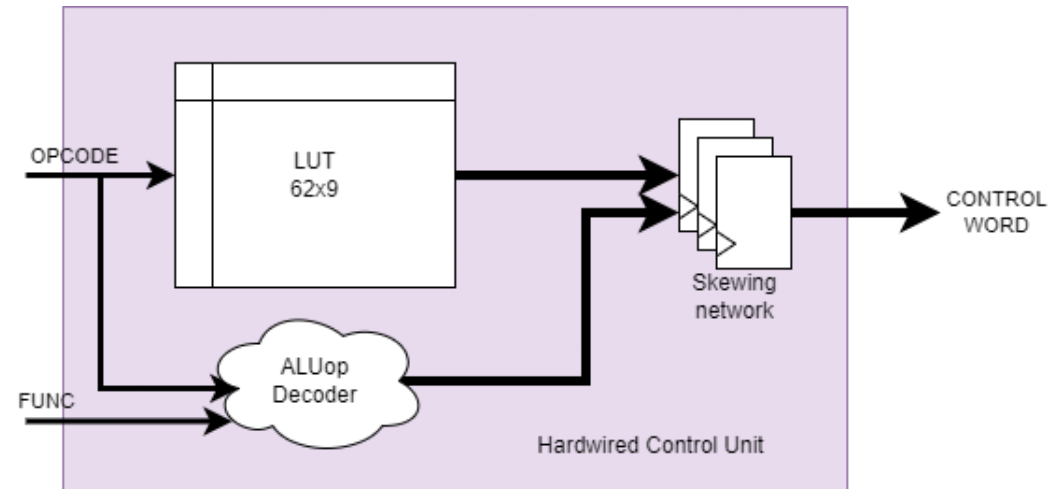
# Control Unit

- LUT size : 62 lines
- Control Word: 9 bits
- Hardwired implementation
- Modular control word generation through **std\_logic\_vector** concatenation to improve readability during debugging phase.


```
--RTYPE Mapping 0x00 --  
std_logic_vector(SEL_REGDST_1 or EN_REGWRITE_1) &      --ID  
std_logic_vector(BRANCH_0 or JUMP_0 or SEL_ALUSRC_0) &  --EX  
std_logic_vector(WE_0 or RE_0) &                        --MEM  
std_logic_vector(SEL_MEMTOREG_0 or SEL_JAL_0),          --WB
```





 
# Simulation – I-type tests

- In order to verify that the instruction set for I-type instructions works, we wrote a simple assembly program that performs:
  - Additions;
  - Subtractions;
  - Mask operations through logical instructions (i.e. AND/OR/XOR etc..).
- Eventually the program halts.



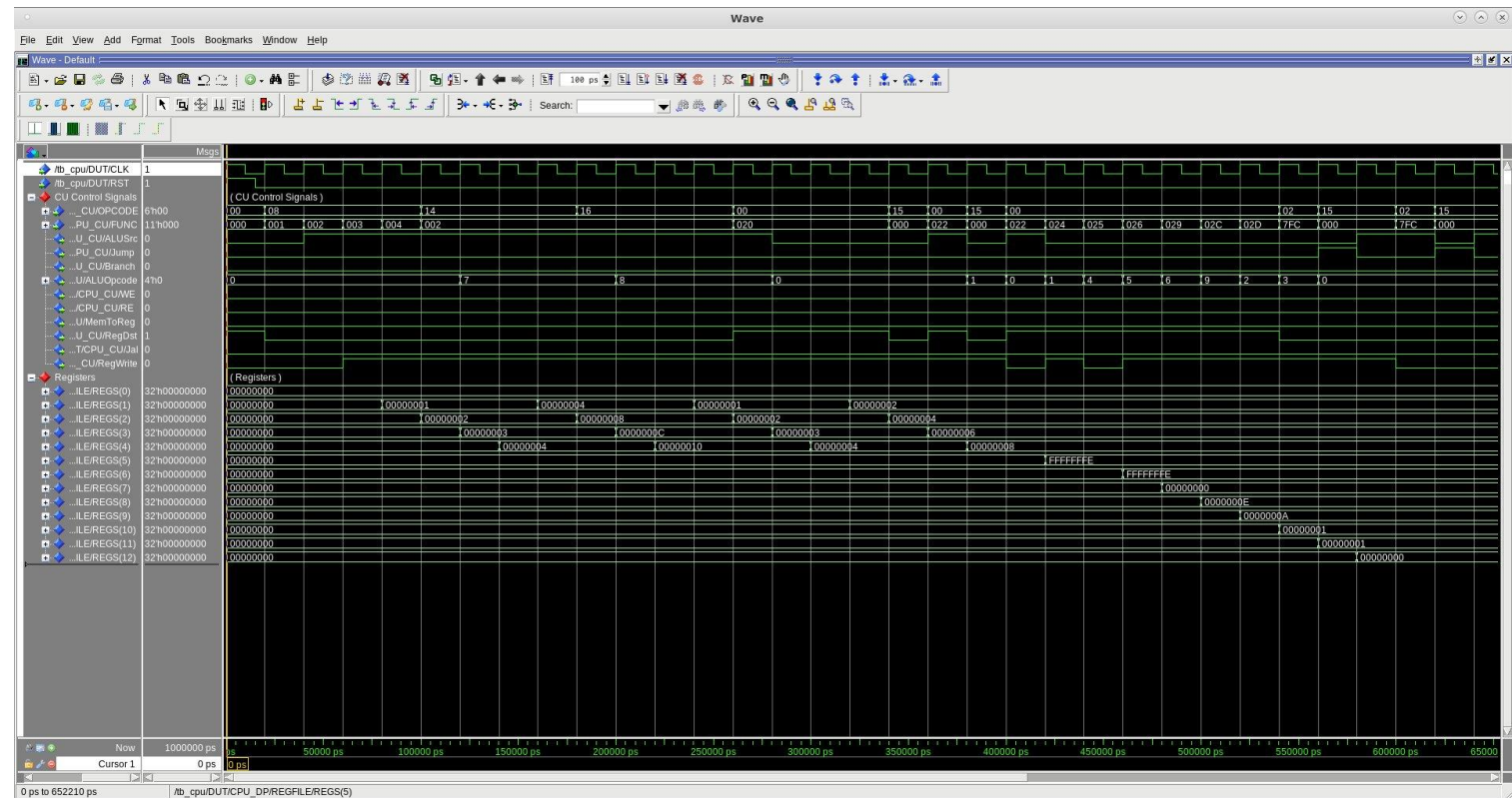
# Simulation – R-type tests

- In order to verify that the instruction set for R-type instructions works, we wrote a simple assembly program that performs:
  - Additions;
  - Subtractions;
  - Shift operations.
- Eventually the program halts.



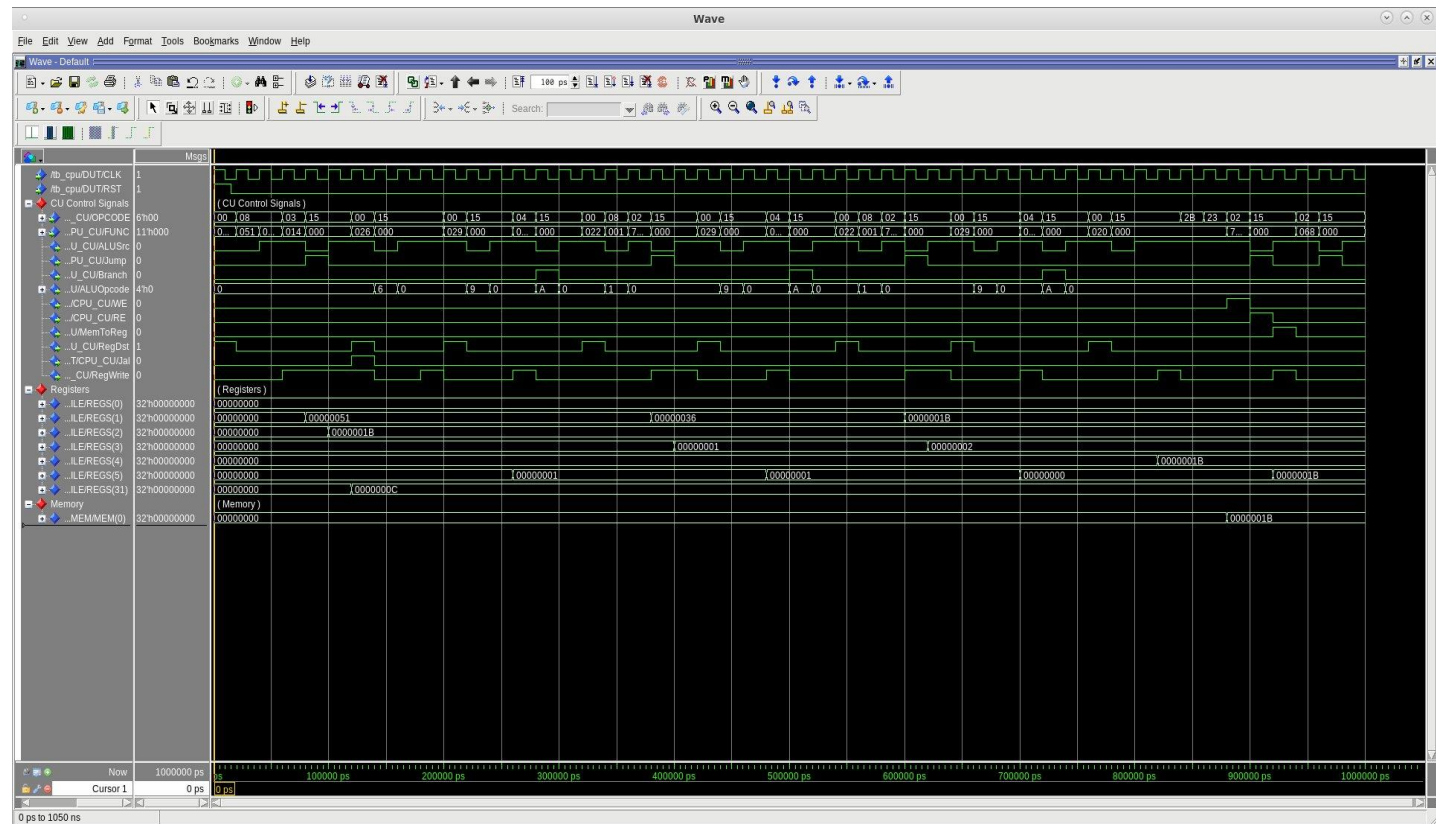
# Simulation – Iterative Division

- In conclusion, to create a more complete program we went through the iterative division simulation.
- The algorithm is executed after a call to a procedure (JAL) and performs 81/27.
- When the procedure ends it stores the result into memory and load again into another register. Then it returns to the caller.
- Eventually the program halts.


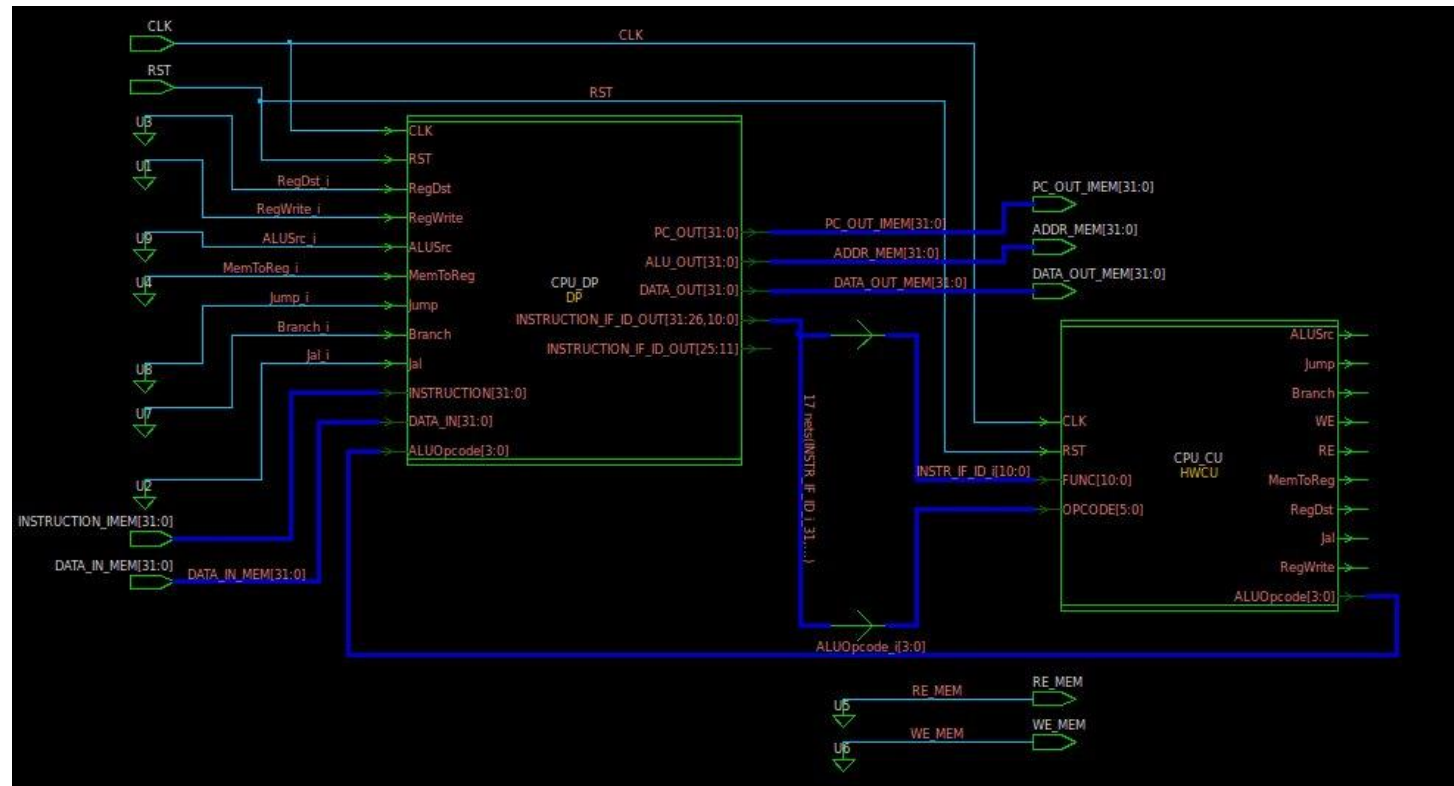
# Synthesis


- Starting from a clock frequency of 50 MHz we reached up to 1 GHz, without major synthesis optimizations.
- Eventually 2 GHz clock frequency goal was achieved using aggressive optimization flow with the usage of **compile\_ultra**, **set\_dont\_touch** to avoid removal of skewing registers and **set\_max\_delay** to constrain the quasi-critical paths.




 
# Physical layout

- We followed the flow for the place & route phase.
- After the post-routing optimization phase, we run a static power analysis and got an estimated power of **500 mW** running at 1 GHz.
- The total power estimated from PrimeTime (1 GHz) was: **426 mW**



# Technical report

---

- The final step was to produce a report describing more in detail what is shown in this presentation.



Politecnico di Torino

Microelectronic Systems

DLX Microprocessor: Design & Development  
Final Project Report

Master degree in Computer Engineering

Referents: Prof. Mariagrazia Graziano, Giovanna Turvani

Authors: group\_38

Alfredo Paolino, Vincenzo Petrolo, Diamante Simone Crescenzo

June 27, 2022

# Possible improvements

---

For a future PRO version, some of the possible improvements:

- Data Hazard Unit
- Branch Prediction Unit
- Floating Point Unit
- Instruction/Data cache
- Extended Instruction set
- Reducing to 1 the Branch delay slot
- Verification using UVM

**Thanks for your attention!**